

**III B. Tech I Semester Regular/Supplementary Examinations, March – 2021****LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **FOUR** Questions from **Part-B**

**PART –A****(14 Marks)**

- 1 a) What is a level translator circuit? Why it is used with the cascaded differential amplifier? [3M]  
 b) What is the major difference between among SSI, MSI, LSI and VLSI ICs? [2M]  
 c) Draw the schematic diagram of an analog multiplier using logarithmic amplifier. [2M]  
 d) How is an op-amp used as a sample and hold circuit? [3M]  
 e) List important features of the 555 timer. [2M]  
 f) Calculate the values of LSB, MSB and full scale output for an 8-bit DAC, if the applied input is in the range of 0-10V. [2M]

**PART –B****(56 Marks)**

- 2 a) Draw the circuit diagram of a basic differential amplifier and explain its transfer characteristics. [7M]  
 b) Draw the circuit diagram of dual input unbalanced output differential amplifier and derive the expression for dc analysis. [7M]
- 3 a) Name the most important parameters of an operational amplifier. What are their ideal values and practical values? [7M]  
 b) Explain dominant pole frequency compensation method. [7M]
- 4 a) What are the advantages of instrumentation amplifier? Derive an expression for the transfer function of an instrumentation amplifier. [7M]  
 b) For the non-inverting a.c amplifier  $R_{in}=50\Omega$ ,  $C_i=0.1\mu f$ ,  $R_I=100\Omega$ ,  $R_F=1k\Omega$  and  $R_O=10k\Omega$ . Determine the gain and bandwidth of the amplifier. [7M]
- 5 a) With a suitable circuit diagram, explain the operation of Narrow band pass filter (NBPF) and give the necessary design expression. [7M]  
 b) Design a wide band-pass filter with  $f_L=200$  Hz.  $F_H=1$  kHz and a pass band gain=4. Draw the frequency response and calculate 'Q' factor for the filter. [7M]
- 6 a) Draw the block diagram of generation of FSK using a PLL. Explain how tracking range affects error voltage in detection? [7M]  
 b) Underline the principle of operation of a Varactor diode and draw the circuit of a VCO using such a diode. [7M]
- 7 a) Define the following terms: [7M]  
 i) Accuracy ii) Resolution iii) Conversion time iv) Percentage resolution.  
 b) Draw the circuit of a ladder type DAC for 4 bits and derive expression for output voltage. [7M]

\*\*\*\*\*

**III B. Tech I Semester Regular/Supplementary Examinations, March – 2021****LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **FOUR** Questions from **Part-B**

**PART -A****(14 Marks)**

- 1 a) What are the four differential amplifier configurations? Which one is not commonly used? [3M]
- b) What are the three operating temperature ranges of the IC? [2M]
- c) Explain the need for emitter resistor  $R_E$  in an emitter coupled astable multivibrator. [3M]
- d) Draw a circuit for multiplication of two analog signals. [2M]
- e) What is the major difference between digital and analog PLLs. [2M]
- f) Define the parameters resolution and settling time of DAC. Obtain the value of resolution for an 8-bit DAC. [2M]

**PART -B****(56 Marks)**

- 2 a) Explain the single input unbalanced output differential amplifier and derive an expression for voltage gain of this differential amplifier. [7M]
- b) Write a short note on cascade differential amplifier stages with suitable circuit diagram. [7M]
- 3 a) Define the terms: CMRR, PSRR, SVRR, Input bias current, Input offset voltage and Gain bandwidth product. [7M]
- b) If an op-amp has a slew rate of  $3 \text{ V}/\mu\text{s}$ , find the rise time for an output voltage of  $12\text{V}$  amplitude resulting from a rectangular pulse input if the op-amp is slew rate limited. [7M]
- 4 a) What are the different modes of operation of an active integrator? Explain them. [7M]
- b) Design a practical integrator circuit to process the sinusoidal input waveform up to  $1\text{KHz}$  and the input amplitude is  $10\text{mV}$ . Assume necessary standard values of resistance. [7M]
- 5 a) Draw the op-amp circuit configuration of a band-pass filter formed by cascading two pole high-pass filters and a two pole low-pass filter, and derive the expression for centre frequency  $f_0$ . [7M]
- b) Describe the working of sample and hold circuit with a suitable diagram. [7M]
- 6 a) Draw the pin diagram of 566 VCO IC and list important specifications of 566 VCO IC. [7M]
- b) Derive an expression for the lock-in range of a PLL? [7M]
- 7 a) Draw the block diagram of a ramp-type digital voltmeter and explain its working. [7M]
- b) Describe the principle of working of an R-2R DAC. What is the minimum and maximum value of gain for it? How can a DAC be used as current-to-voltage converter? [7M]

\*\*\*\*\*

**III B. Tech I Semester Regular/Supplementary Examinations, March – 2021**  
**LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **FOUR** Questions from **Part-B**

**PART –A**


(14 Marks)

- 1 a) Why is a cascaded configuration used in an op-amp? [2M]
- b) What are the advantages of using a schematic symbol for an op-amp? [3M]
- c) Describe the operation of zero-crossing detector. [3M]
- d) What is an all-pass filter? Where and why it is needed? [2M]
- e) What is a capture range and lock range of PLL? [2M]
- f) Define important performance specifications of Digital to Analog converters listing their typical values. [2M]

 **PART –B**

(56 Marks)

- 2 a) Mention the types of open loop configurations of an Op-Amp. Explain each configuration in detail. [7M]
- b) Draw the ac and dc equivalent circuits of single input balanced output differential amplifier and also derive an expression for voltage gain of this differential amplifier. [7M]
- 3 a) Derive CMRR of emitter coupled differential amplifier. What do you mean by difference mode gain? [7M]
- b) For an OP-AMP, PSRR is 70dB, CMRR is  $10^5$ , and differential mode gain is  $10^5$ . The output voltage changes by 20V in 4  $\mu$ s. Calculate:  
 i) Numerical value of PSRR, ii) Common mode gain, iii) Slew rate. [7M]
- 4 a) Explain the operation of a practical differentiator. Use relevant expressions, diagrams. [7M]
- b) In the below circuit, it can be shown that  $V_0 = \alpha_1 V_1 + \alpha_2 V_2 + \alpha_3 V_3$ . Find the values of  $\alpha_1$ ,  $\alpha_2$ ,  $\alpha_3$ . Find the value of  $V_0$  if  
 i)  $R_4$  is Short circuited ii)  $R_4$  is removed iii)  $R_1$  is short circuited. [7M]



- 5 a) Describe the principle of operation of an inverting first order low-pass filter using op-amp and draw its frequency response curve. [7M]
- b) Design a second order Butter-worth low pass filter having a cut-off frequency of 1KHz. The damping factor is equal to 1.414. [7M]

Code No: R1631042

**R16**

**SET - 3**

- 6 a) Draw the dc voltage versus phase difference characteristics of balanced modulator phase detector of a PLL indicating all important regions. [7M]  
b) With a neat functional diagram, explain the operation of VCO and also derive an expression for free running frequency,  $f_0$ . [7M]
- 7 a) Using a neat sketch, explain the working of a parallel comparator ADC. [7M]  
b) Draw the circuit of a Weighted Resistor DAC and obtain expression for n-bits. [7M]

\*\*\*\*\*

**2 of 2**



**III B. Tech I Semester Regular/Supplementary Examinations, March – 2021****LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **FOUR** Questions from **Part-B**

**PART –A****(14 Marks)**

- 1 a) Explain why open-loop op-amp configuration is not used for linear applications? [2M]
- b) What is the difference between monolithic and hybrid ICs? [2M]
- c) Explain the working principle of a feedback limiter circuit. [2M]
- d) Define a filter. How are filters classified? [3M]
- e) For being used in a PLL, describe the characteristics that a VCO must possess. [3M]
- f) Compare Successive approximation A/D converter with Parallel comparator type A/D converter. [2M]

**PART –B****(56 Marks)**

- 2 a) With suitable circuit diagram, explain about Dual input balanced output differential amplifier. And derive necessary expressions for dc and ac analysis. [7M]
- b) What is a differential amplifier? Mention the classification of differential amplifier with neat diagrams. [7M]
- 3 a) What is an Op-Amp? Draw the functional block diagram of an Op-Amp and explain each block in detail. [7M]
- b) An op-amp has a slew rate of  $2V/\mu s$ . What is the maximum frequency of an output sinusoid of peak value 5V at which the distortion sets in due to the slew rate limitation? [7M]
- 4 a) Using three op-amps draw the circuit diagram of an instrumentation amplifier and derive an expression for the output voltage. [7M]
- b) Design a single op-amp logarithmic amplifier and derive the relation between the output and input voltage? Explain why it is called a logarithmic amplifier? [7M]
- 5 a) Draw a band pass filter circuit with its frequency response curve. Explain its working. [7M]
- b) Using an op-amp, design a second order low-pass filter with a cutoff frequency of 1KHz. [7M]
- 6 a) Draw the circuit diagram of a 555 timer connected as an astable multivibrator and explain its operation. [7M]
- b) Using 555 timers, design a monostable multivibrator to produce pulses of width of 110 msec. Use a  $1\mu F$  capacitor. [7M]
- 7 a) Draw and explain the block diagram of a counter type ADC and list out its disadvantages. [7M]
- b) Draw the simplified block diagram of a successive approximation ADC and explain its working. [7M]

\*\*\*\*\*