

III B. Tech I Semester Supplementary Examinations, October/November - 2020**LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A**(14 Marks)**

1. a) What is the significance of Level translator? [2M]
- b) Define Drift and give its ideal and practical values. [2M]
- c) Draw the V to I convertor. [2M]
- d) What is an all-pass filter and Notch Filter? [3M]
- e) List the applications of PLL. [3M]
- f) What are the advantages of analog to digital conversion? [2M]

PART -B**(56 Marks)**

2. a) Draw the circuit diagram of differential amplifier with dual input and balanced output. Derive the expressions for differential gain A_d , input resistance R_i , and output resistance R_o . [7M]
- b) Write and explain about DC coupling and cascaded differential amplifier stages. [7M]
3. a) List out the applications and Temperature ranges of IC 741 Op-amp. [7M]
- b) List out the DC characteristics of Op-amp and Explain. [7M]
4. a) For the given output expression design an adder circuit using an Op-Amp: [7M]

$$V_o = -(0.1V_1 + V_2 + 10V_3)$$
- b) With a neat sketch explain the operation of Anti log Amplifiers and derive its output voltage in detail. [7M]
5. a) Design a second order butter worth low pass filter having an upper cut off frequency of 2 KHz. [7M]
- b) With a neat sketch explain the operation of IC 1496 balanced modulator. [7M]
6. a) Explain the working of Astable multivibrator using 555 Timer with relevant circuits and waveforms. [7M]
- b) With a neat sketch, explain IC566 VCO operation and discuss any two applications. [7M]
7. a) With a neat Sketch explain the R-2R ladder resistor type DAC. [8M]
- b) Define the following terms as related to ADC: [6M]
 - i) Conversion time
 - ii) Percentage resolution
 - iii) Linearity.

