

II B. Tech I Semester Supplementary Examinations, October/November - 2020
SWITCHING THEORY AND LOGIC DESIGN
 (Com to ECE, EIE and ECC)


Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A

 1. a) Express decimal digits 0-9 in BCD code and 2 4 2 1 code. (2M)
- b) Implement the function $F(x, y, z) = \sum(0, 6)$ with NAND gates. (3M)
- c) For the figure given, the output will be. (3M)



- d) Explain basic structure of PAL. (2M)
- e) Convert JK Flip Flop to D Flip Flop. (2M)
- f) Explain the representation of State Diagram in detail. (2M)

PART -B

2. a) What is a reflected code? Write about reflected codes by giving examples. (7M)
- b) Design BCD code to Gray code converter. (7M)
3. a) Obtain the simplified expressions in sum of products for the following Boolean functions using Karnaugh-Map. (7M)
 - i) $F(A, B, C, D) = \sum(7, 13, 14, 15)$
 - ii) $F(w, x, y, z) = \sum(2, 3, 12, 13, 14, 15)$
- b) Minimize the following Boolean expressions to the required no. of literals (7M)
 - i) $BC + AC' + AB + BCD$ to four literals
 - ii) $ABC + A'B'C + A'BC + ABC' + A'B'C'$ to five literals
4. a) Derive Boolean expression for a 2input Ex-OR gate to realize with 2 input NAND gates without using complemented variables and draw the circuit. (7M)
- b) Redraw the given circuit in (figure4) after simplification. (7M)

 


Figure 4

5. a) For the given 3-input, 4-output truth table of a combinations circuit, tabulate the PAL programming table for the circuit. (7M)

Inputs			Output			
x	y	z	A	B	C	D
0	0	0	1	0	0	
0	0	1	1	1	1	
0	1	0	1	0	1	
0	1	1	0	1	0	
1	0	0	1	0	1	
1	0	1	0	0	0	1
1	1	0	1	1	1	
1	1	1	0	1	1	

- b) Derive the PLA programming table for the combinational circuit that squares a 3 bit number. (7M)
6. a) What is flip-flop? How can be used in sequential circuit and explain in detail. (7M)
- b) Explain about Master-slave flip-flop in detail. (7M)
7. a) The output Z of a fundamental mode, two input sequential circuit is to change from 0 to 1 only when x2 changes from 0 to 1 while x1=1. The output changes from 1 to 0 only when x1 changes from 1 to 0 while x2=1. Find a minimum row reduced flow table. (7M)
- b) Draw the state diagrams of a sequence detector which can detect 101. (7M)