

II B. Tech II Semester Supplementary Examinations, November - 2018**PULSE AND DIGITAL CIRCUITS**

(Com to ECE, EIE, ECC)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B****PART -A**

1. a) If Pulse input is applied to a RC differentiator circuit ,What is the output signal and draw the wave form? 3M
- b) If $R_f=400\Omega$, $R_r=40K\Omega$, Find 'R' of a Clamping Circuit? 2M
- c) If reverse recovery time of a diode is 10 nsec, find f_{max} ? 2M
- d) Calculate the width of hysteresis if $UTP=7V$ and $LTP=6.5V$ 2M
- e) Define voltage time base generator? 2M
- f) What is meant by pedestal in sampling gate? 3M

PART -B

2. a) The limited ramp is applied to a RC differentiator circuit. Draw the Waveforms for the case, i) $T=0.2RC$ ii) $T=RC$ and iii) $T=5RC$. 7M
- b) Explain the response of RLC series circuit for step input with suitable waveforms? 7M
3. a) Design and explain the clipper circuit using two -Zener diodes? 7M
- b) Classify the clamper circuit and explain any of the circuit? 7M
4. a) Explain the behavior of BJT as a switch. Give applications. 7M
- b) With suitable diagram explain the function of a basic bistable multivibrator? List out the drawbacks with this circuit? 7M
5. a) Determine the period and frequency of Oscillation for an astable multivibrator With component values $R_1= 2K\Omega$, $R_2=10 K\Omega$, $C_1=0.01\mu F$ and $C_2=0.05\mu F$. 7M
- b) With the help of circuit diagram ,explain the working of collector coupled Monostable multivibrator. 7M
6. a) Draw a simple single stage transistor miller integration circuit and explain How it behaves as a time-base circuit. 7M
- b) Draw the circuit of transistorized bootstrap generator and explain its working? 7M
7. a) State the two basic types of sampling gates and explain them 7M
- b) List the advantages and disadvantages of RTL family. 7M

